
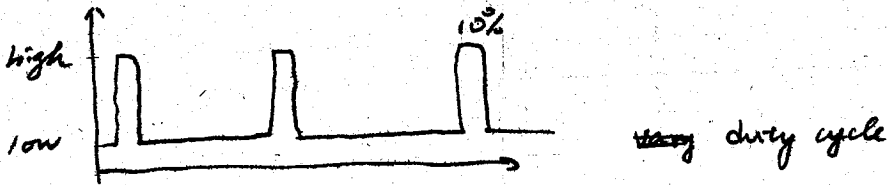


PWM (Pulse Width Modulation)

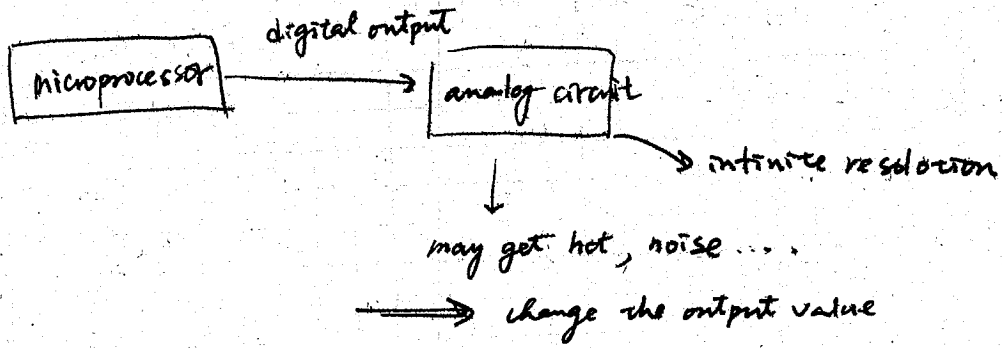


ex) 9 Volt battery to a light bulb

50 ms on  
50 ms off

50% duty cycle → bulb feels it were connected to a 4.5 V battery

H-bridge

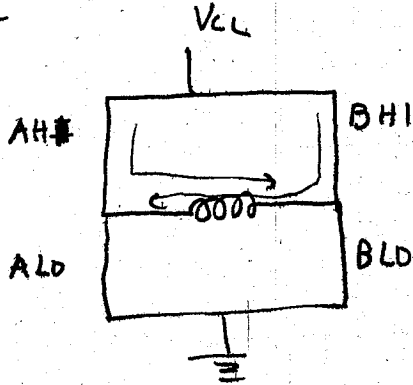


current can go either way  
to the motor by controlling  
the on-offs of AH, AL, BH, BL


- bi-directional current switch with intrinsic protection diodes
- current sensing LMD18200
- over current protection
- thermal warning / shut down
- speed / magnitude control
- Braking
- application examples

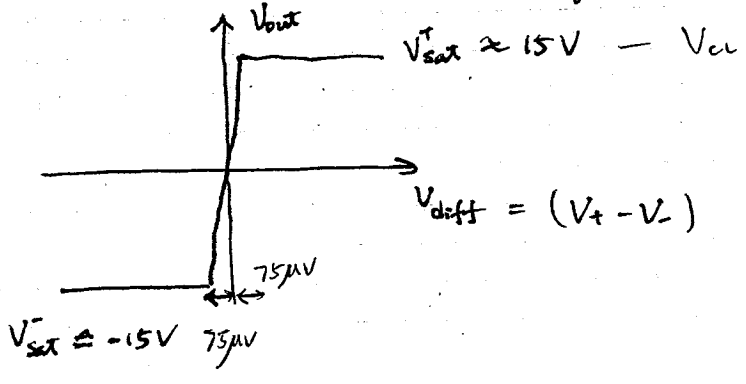22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS  
AMPAD

• Op (operation amplifier) working area ~~area~~  
 saturating




• Comparator

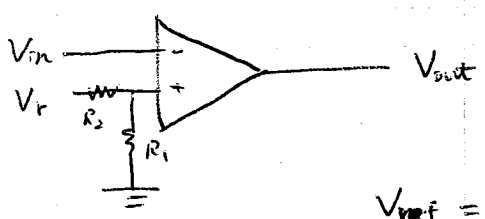

$$V_{ref} = V_r \cdot \frac{R_1}{R_1 + R_2}$$

When  $V_{in} > V_{ref} \rightarrow V_{out} \approx -15V$

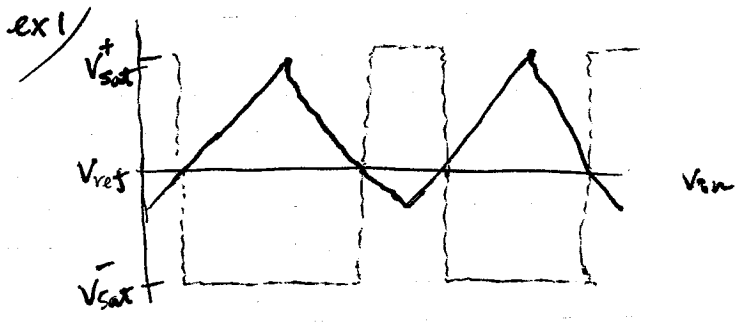$V_{in} < V_{ref} \rightarrow V_{out} \approx 15V$



ex2/ Air conditioner

temperature  $\rightarrow$  voltage  $\rightarrow V_{in} \rightarrow ?^\circ C$

$V_{ref} = 28^\circ C$

open & close all the time

(how to solve it?)

22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS




# Schmitt Trigger $\rightarrow$ comparator with hysteresis

Comparator




$$V_{in} > V_{ref} \rightarrow V_{out} = V^+$$

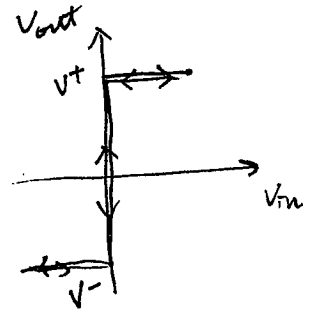
$$V_{in} < V_{ref} \rightarrow V_{out} = V^-$$



problem

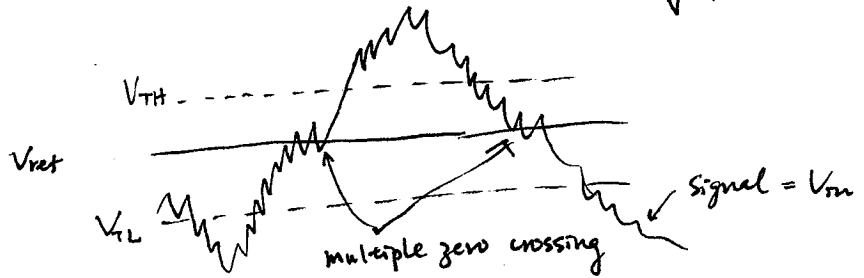

## Schmitt Trigger (bistable circuit)

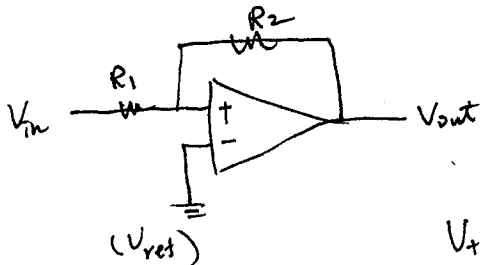

$$V_+ = ?$$

$$\frac{V_{in} - V_+}{R_1} = \frac{V_+ - V_{out}}{R_2}$$

$$\Rightarrow V_+ \text{ from } \begin{matrix} \text{positive} \\ \text{negative} \end{matrix} \text{ to just pass } 0, \text{ before passing } 0 \Rightarrow V_+ = V_{out} \frac{R_1}{R_1 + R_2} + V_{in} \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow V_+ > 0 \Rightarrow V_{out} = V^+$$

$$\Rightarrow \text{by setting } V_+ \approx 0, V_{out} = V^+ \Rightarrow V_{in} = -V^+ \frac{R_1}{R_2} = V_{TL}$$

$$\Rightarrow \text{afterwards } V_+ < 0, V_{out} = V^- \text{ and continue to be } V^- \text{ for } V_+ < 0$$

$\Rightarrow$  On the other hand

$$\Rightarrow V_+ \text{ from negative to just pass } 0, \text{ before passing } 0$$

$$\Rightarrow V_+ < 0 \Rightarrow V_{out} = V^-$$

$$\Rightarrow \text{by setting } V_+ \approx 0, V_{out} = V^- \Rightarrow V_{in} = -V^- \frac{R_1}{R_2} = V_{TH}$$

$$\Rightarrow \text{afterwards } V_+ > 0, V_{out} = V^+ \text{ and continue to be } V^+ \text{ for } V_+ > 0$$

the state will maintain between  $V_{TL}$  &  $V_{TH}$

$\Rightarrow$  bistable with hysteresis

$\Rightarrow$  Schmitt trigger

